



The Single PS Voltage Long Tailed Phase Splitter. This circuit forgoes the use of a negative PS. Instead, it relies on DC coupling at the input to a high voltage to bias up the circuit.

Tube

Tube = 6SN7
 Number = 1
 mu = 20
 gm = 2.6 ma/v
 rp = 7700 ohm
 I_{max} = 20 ma
 V_{max} = 450 v
 W_{max} = 3.75 w
 C_{gp} = 4 pf

Circuit Setup

R_k = 12 k
 R_{in} = 1 k
 R_L = 110 k
 R_a = 22 k
 Cap = 1μf
 I = 9ma
 V B+ = 400v

AC Results

Gain = 7.39	Gain dB = 17.4 dB
Phase = both	PSRR = -0.306 dB
Z input = 269 k	Z output = 5.42 k
F -3dB low = 1.38 hz	F -3dB high = > 1 mhz
Balance = 9.36%	Gain@T2 = 16.5 dB

DC Results

V tube = 193 v	V _{Ra} = 99 v
V _{bias} = -6.93 v	V _{g DC} = 101 v
V _{th} = 5.86 v	V _{max out} = -51/+51.2 v
Plate Dis. = 868 mw	Total Dis. = 4.46 w
R _a Dis. = 445 mw	W R _k = 486 mw

Calculated Part Values

R _{a2} = 24.9 k	R _{a2} -R _a = 2.8 k
--------------------------	---